

Western New England University
College of Engineering
ECE Department
Microwave Engineering
EE 414/514
Spring 2024
Design Project #4
Due: April 26, 2024

Name: Nittala Satya Surya Lakshmi Vasuki Siva Srinivas
#Id – 620094
#Email – sn620094@wne.edu

References: _____

Design Project #4

	Score	Max
Butterworth Matching Network Design		200
Butterworth MATLAB Simulation		100
Chebyshev Matching Network Design		200
Chebyshev MATLAB Simulation		100
ADS (Microstrip TRLs)		100
ADS (Microstrip TRLs SD)		100
Summary Graphs		100
Presentation		100
Total		1000

1. Design a Butterworth multi-section transformer to match a $100\text{-}\Omega$ load ($R_L = 100\ \Omega$) to a $50\text{-}\Omega$ generator ($R_g = 50\ \Omega$).
 - The center frequency is 8 GHz ($f_0 = 8\ \text{GHz}$).
 - The bandwidth must be greater than or equal to 6.4 GHz ($BW_f \geq 6.4\ \text{GHz}$).
 - The return loss must be greater than or equal to 30 dB ($RL \geq +30\ \text{dB}$ or $|S_{11}| \leq -30\ \text{dB}$) over the bandwidth.
2. Using MATLAB, simulate the matching network designed in Task (1). Employ ideal transmission lines and a frequency range of 0 to 16 GHz. In addition, employ “driveway transmission lines” at the input and output with an electrical length of 90° . Determine the actual bandwidth (in GHz) for which the input return loss is greater than or equal to 30 dB ($RL \geq +30\ \text{dB}$ or $|S_{11}| \leq -30\ \text{dB}$).
 - Determine a value for S_{11} , S_{21} , S_{12} , and S_{22} at 8 GHz.
3. Design a Chebyshev multi-section transformer to match a $100\text{-}\Omega$ load ($R_L = 100\ \Omega$) to a $50\text{-}\Omega$ generator ($R_g = 50\ \Omega$).
 - The center frequency is 8 GHz ($f_0 = 8\ \text{GHz}$).
 - The bandwidth must be greater than or equal to 6.4 GHz ($BW_f \geq 6.4\ \text{GHz}$).
 - The return loss must be greater than or equal to 30 dB ($RL \geq +30\ \text{dB}$ or $|S_{11}| \leq -30\ \text{dB}$) over the bandwidth.
4. Using MATLAB, simulate the matching network designed in Task (3). Employ ideal transmission lines and a frequency range of 0 to 16 GHz. In addition, employ “driveway transmission lines” at the input and output with an electrical length of 90° . Determine the actual bandwidth (in GHz) for which the input return loss is greater than or equal to 30 dB ($RL \geq +30\ \text{dB}$ or $|S_{11}| \leq -30\ \text{dB}$).
 - Determine a value for S_{11} , S_{21} , S_{12} , and S_{22} at 8 GHz.
5. Using ADS, simulate the matching network designed in Task (3). Employ microstrip transmission lines and a frequency range of 0 to 16 GHz. In addition, employ “driveway transmission lines” at the input and output with an electrical length of 90° . Assume that the microstrip transmission lines are to be realized using a 0.635 mm thick Duroid 6010 substrate ($\epsilon_r = 10.7$, $\tan \delta = 0.0023$, $\sigma_c = 5.8 \times 10^{-7}\ \text{S/m}$, and $t = 18\ \mu\text{m}$).
 - Determine a value for S_{11} , S_{21} , S_{12} , and S_{22} at 8 GHz.
6. Add the microstrip step element (MSTEP) to the model in Task (5).
 - Determine a value for S_{11} , S_{21} , S_{12} , and S_{22} at 8 GHz.

7. Summarize the results.
 - On the same graph, plot $|S_{11}|$ (in dB) for the Butterworth simulated using MATALB and the Chebyshev simulated using MATALB. Employ a domain of 0 to 16 GHz and a range of -40 to 0 dB.
 - On the same graph, plot $|S_{21}|$ (in dB) for the Butterworth simulated using MATALB and the Chebyshev simulated using MATALB. Employ a domain of 0 to 16 GHz and a range of -0.25 to 0 dB.
 - On the same graph, plot $|S_{11}|$ (in dB) for the Chebyshev simulated using MATALB, ADS (Microstrip TRLs), and ADS (Microstrip TRLs with SD). Employ a range of -40 to 0 dB.
 - On the same graph, plot $|S_{21}|$ (in dB) for the Chebyshev simulated using MATALB, ADS (Microstrip TRLs), and ADS (Microstrip TRLs with SD). Employ a domain of 0 to 16 GHz and a range of -0.45 to 0 dB.
8. Present the results from the design project into a well-organized presentation.

Design Project - 4

By: Nittala Satya Surya Lakshmi Vasuki Siva Srinivas

#Id – 620094

Email – sn620094@wne.edu

Butterworth Matching Network Design

Butterworth Matching Network Design MATLAB Calculations


```
new_fL = 4.5974 GHz
new_fH = 11.4026 GHz
wzi = (1.0000 < +180.0000°)
w = (1.0000 < -126.7597°)


-----
Gamma_k( 1) = 0.0108
Gamma_k( 2) = 0.0542
Gamma_k( 3) = 0.1083
Gamma_k( 4) = 0.1083
Gamma_k( 5) = 0.0542
Gamma_k( 6) = 0.0108

z1 = 51.0949 Ohms
z2 = 56.9394 Ohms
z3 = 70.7107 Ohms
z4 = 87.8126 Ohms
z5 = 97.8572 Ohms
z6 = 100.0000 Ohms

S21_min (RL) = 0.9995 W/W
S21_min (RL) = -0.0043 dB
Ap (RIPPLE) = 0.0043 dB
>> wz1
```

k	0	1	2	3	4	5	6
Z_k	50.0000	51.0949	56.9394	70.7107	87.8126	97.8572	100.0000
Γ_k	0.0108	0.0542	0.1083	0.1083	0.0542	0.0108	-----

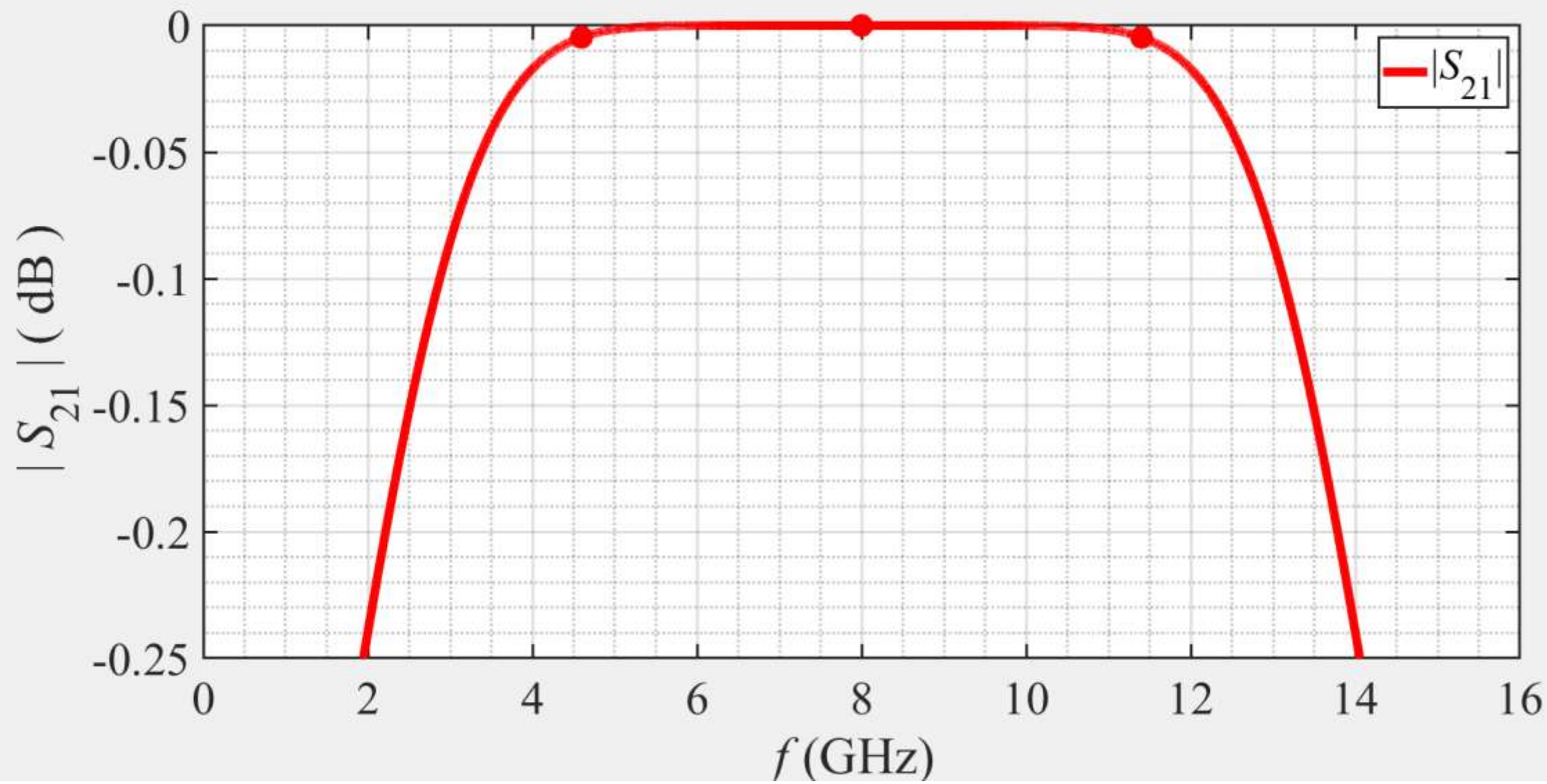

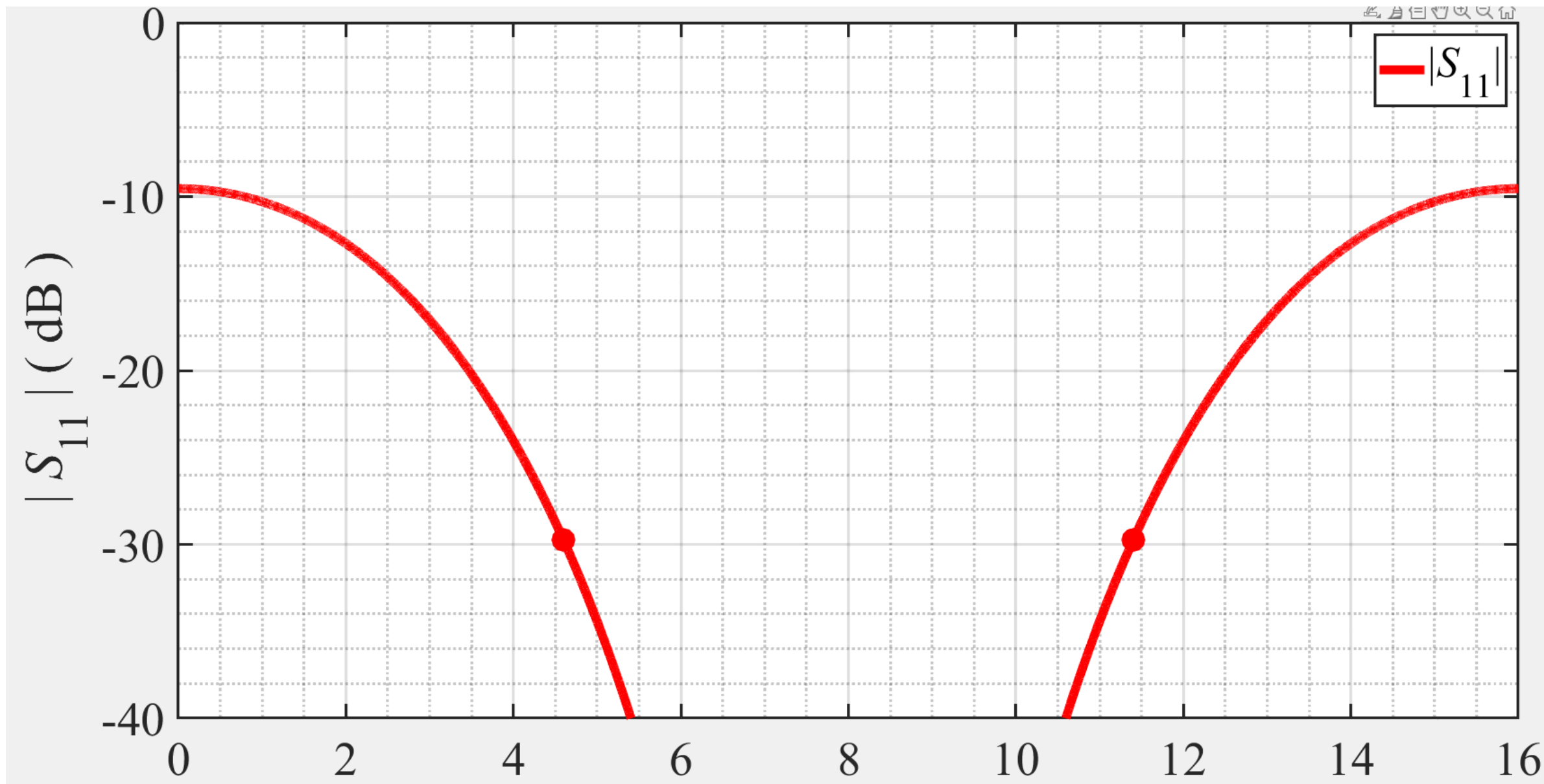

Chebyshev Matching Network Design

Chebyshev Matching Network Design MATLAB Calculations

```
new_fL = 4.5021 GHz
new_fH = 11.4979 GHz
uz( 1) = -0.8660
uz( 2) = 0.0000
uz( 3) = 0.8660

T_N( 1) = 4.0000
T_N( 2) = 0.0000
T_N( 3) = -3.0000
T_N( 4) = 0.0000

Uz_poly( 1) = -0.8660
Uz_poly( 2) = 0.0000
Uz_poly( 3) = 0.8660

wzi( 1) = (1.0000 < +113.3866°)
wzi( 2) = (1.0000 < +180.0000°)
wzi( 3) = (1.0000 < -113.3866°)

Ik( 1) = 1.0000
Ik( 2) = 1.7939
Ik( 3) = 1.7939
Ik( 4) = 1.0000


Gamma_k( 1) = 0.0620
Gamma_k( 2) = 0.1113
Gamma_k( 3) = 0.1113
Gamma_k( 4) = 0.0620


Z1 = 56.6125 Ohms
Z2 = 70.7874 Ohms
Z3 = 88.5115 Ohms
Z4 = 100.2171 Ohms

S21_min (RL) = 0.9995 W/W
S21_min (RL) = -0.0043 dB
Ap (RIPPLE) = 0.0043 dB
>>
```

i	u_{zi}	θ_{zi}	w_{zi}
1	-0.8660	123.3067	(1.0000 < +113.3866°)
2	0.0000	90.0000	(1.0000 < +180.0000°)
3	0.8660	56.6933	(1.0000 < -113.3866°)

k	0	1	2	3	4	
I_k	1.0000	1.7939	1.7939	1.0000		
Γ_k	0.0620	0.1113	0.1113	0.0620	-----	
Z_k	50.0000	56.6125	70.7874	88.5115	100.2171	Ohms

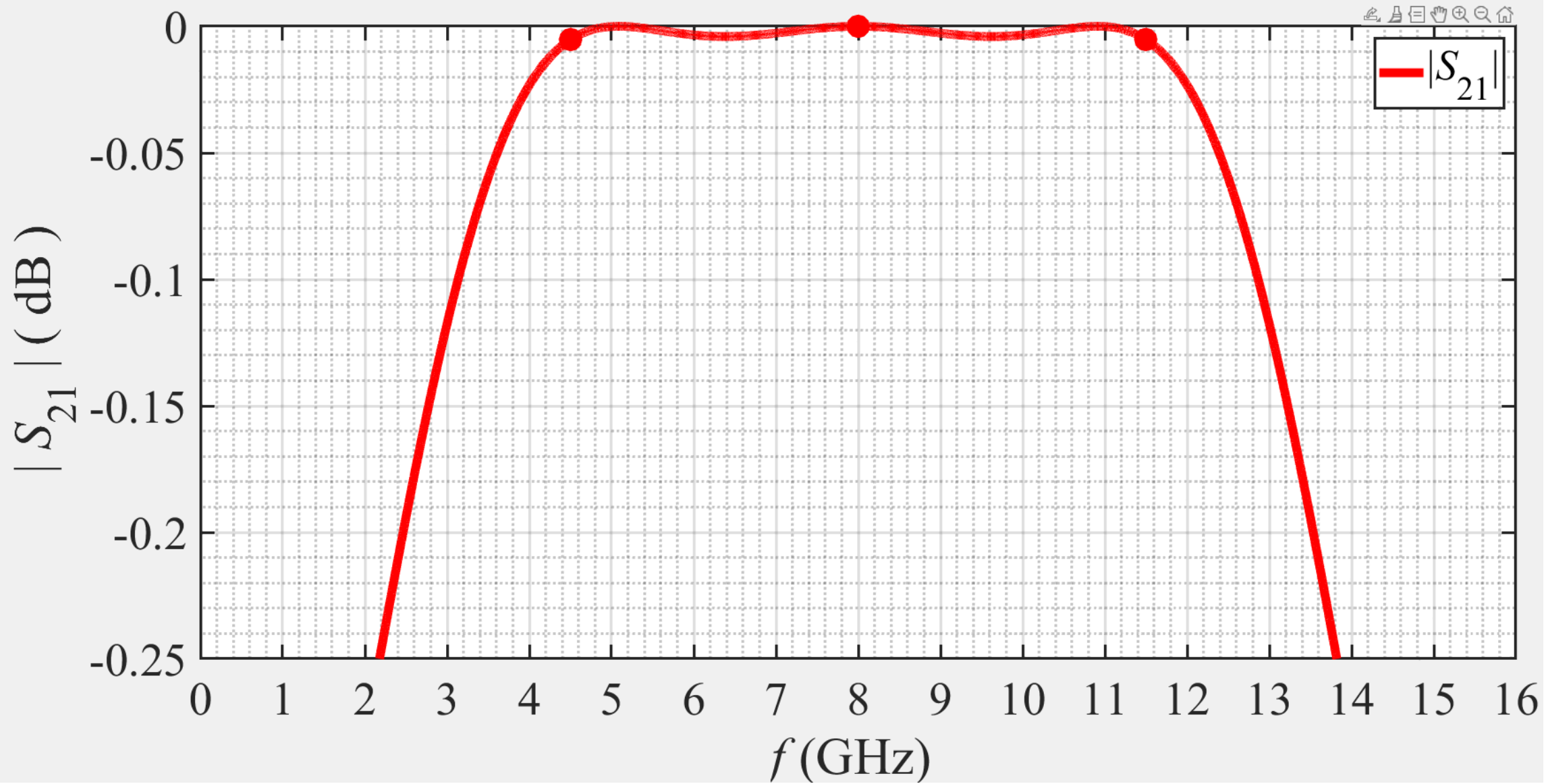

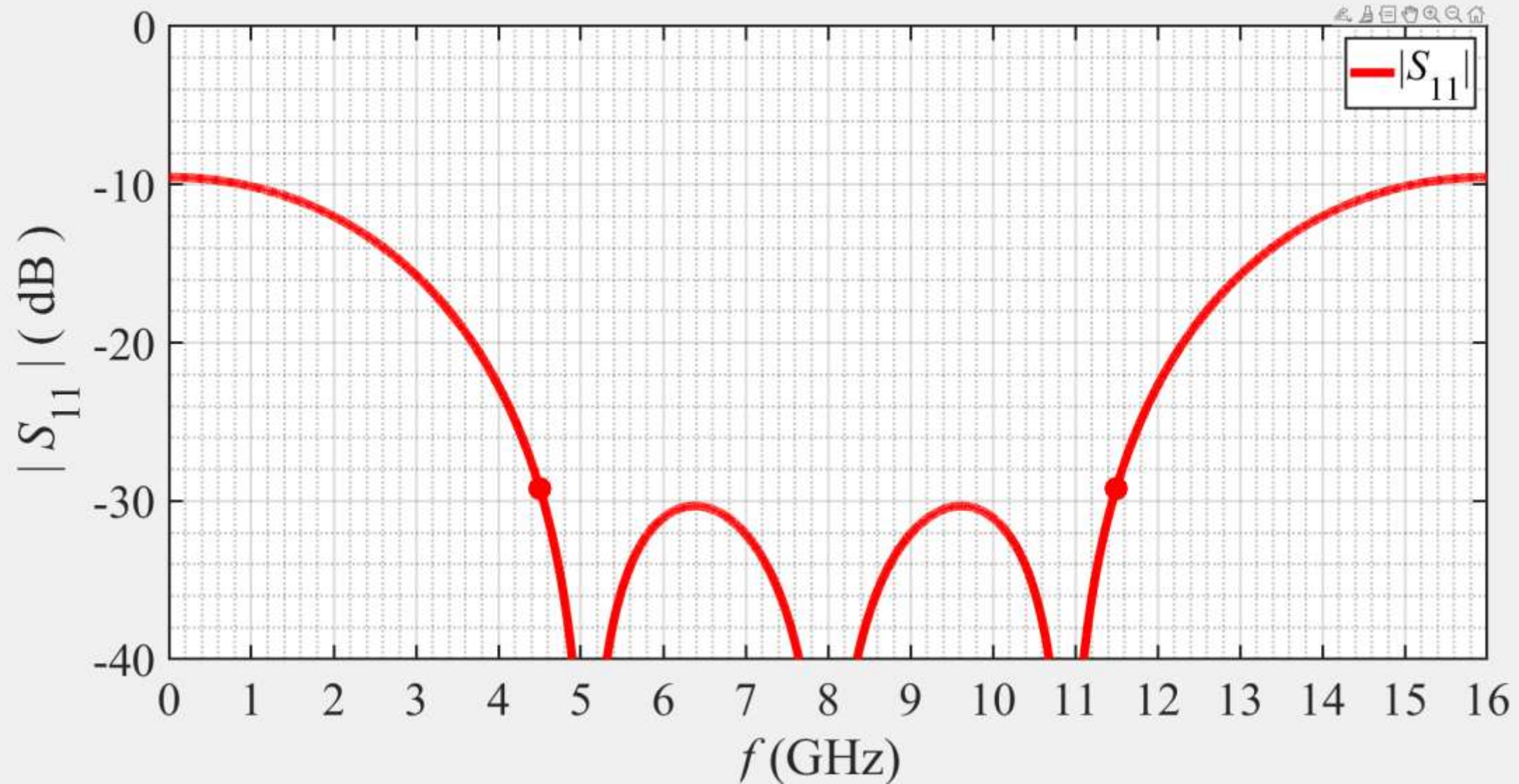

ADS (Microstrip TRLs)


 S-PARAMETERS

S_Param
SP1
Start=0 GHz
Stop=16 GHz
Step=0.03 GHz

DisplayTemplate
disptemp1
"S_Params_Quad_dB_Smith"


MSub

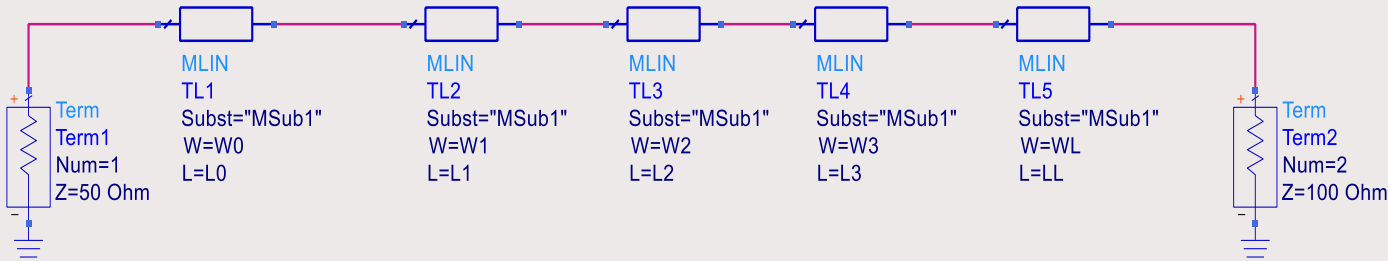MSUB
MSub1
H=0.635 mm
Er=10.7
Mur=1
Cond=5.8e+7
Hu=1e+33 mm
T=18 um
TanD=0.0023
Rough=
Bbase=
Dpeaks=







VAR
VAR1
W0=0.554162 mm
L0=3.490710 mm
W1=0.415484 mm
L1=3.541880 mm
W2=0.224515 mm
L2=3.634570 mm
W3=0.101513 mm
L3=3.735550 mm
WL=0.058710 mm
LL=3.798950 mm

ADS (Microstrip TRLs) Layout

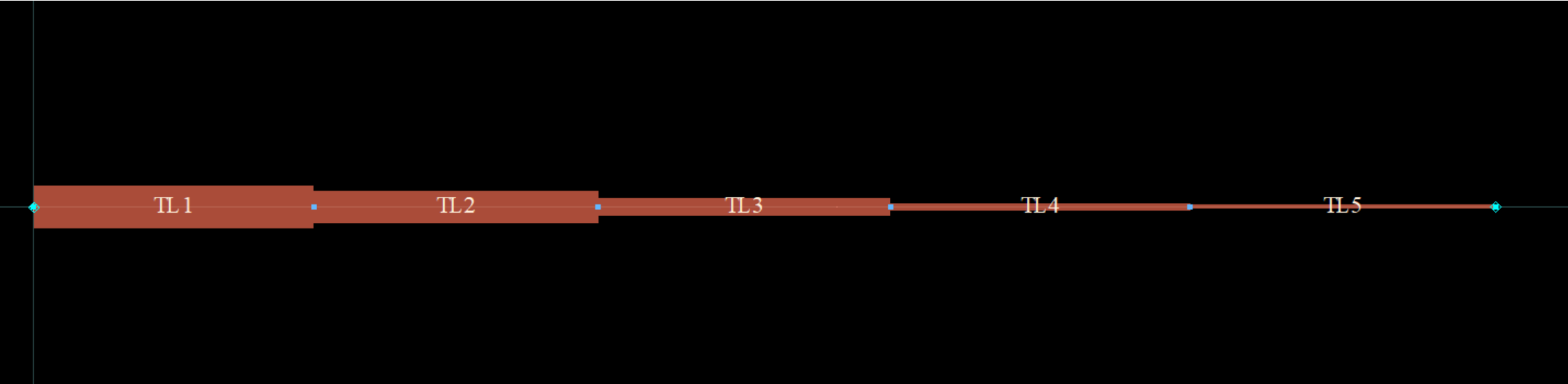

ADS (Microstrip TRLs)

S-Parameters vs. Frequency

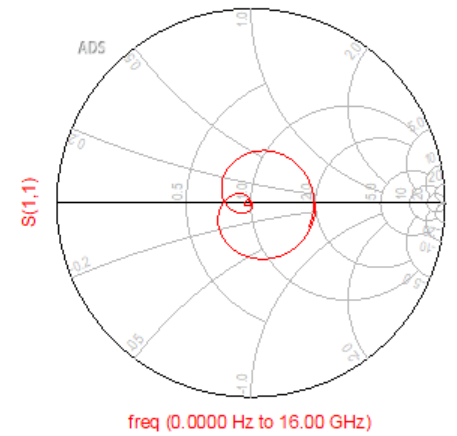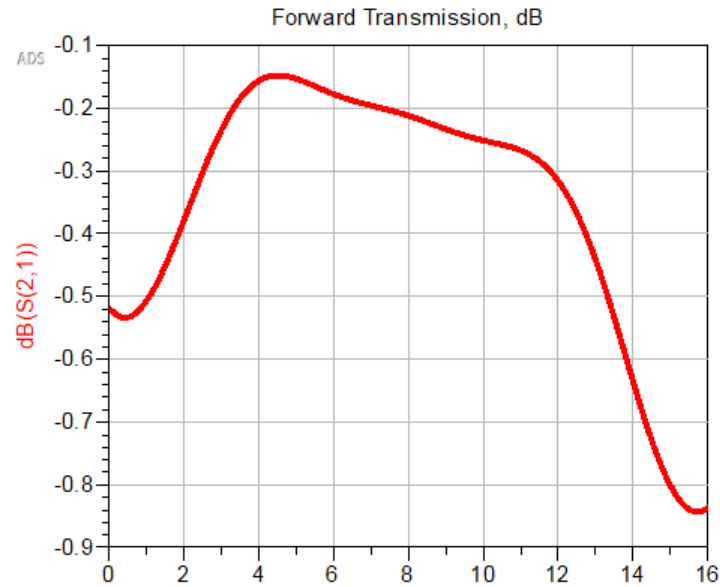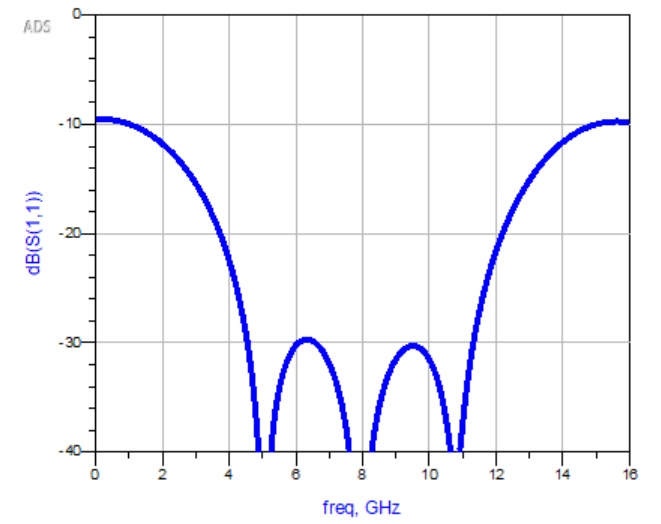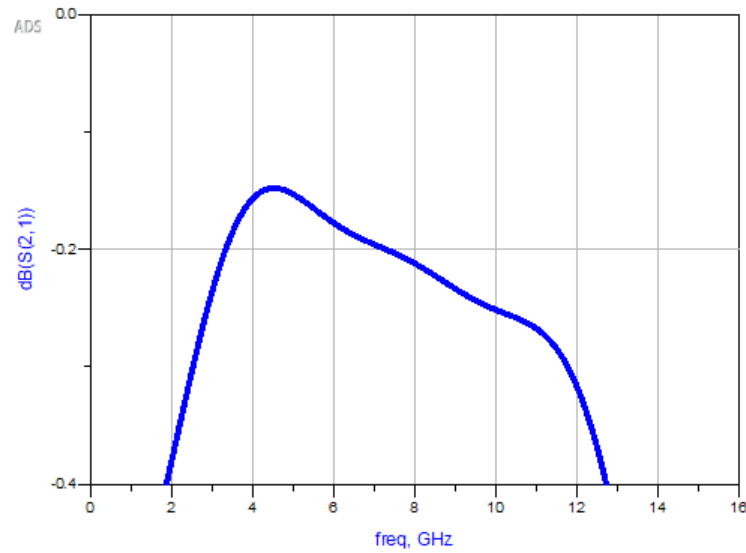

ADS -Microstrip TRLs(MSTEP)

 S-PARAMETERS


S_Param
SP1
Start=0 GHz
Stop=16 GHz
Step=0.03 GHz

Disp
Temp

DisplayTemplate
disptemp1
"S_Params_Quad_dB_Smith"

MSub

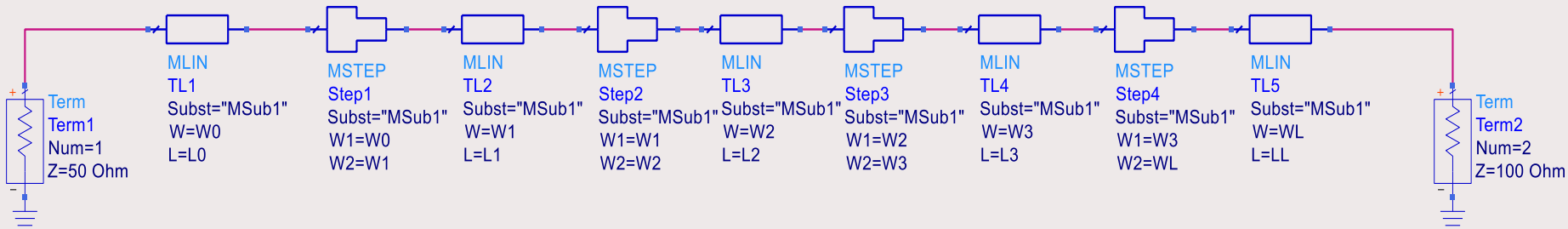
MSUB
MSub1
H=0.635 mm
Er=10.7
Mur=1
Cond=5.8e+7
Hu=1e+33 mm
T=18 um
TanD=0.0023
Rough=
Bbase=
Dpeaks=



Var
Eqn





VAR
VAR1
W0=0.554162 mm
L0=3.490710 mm
W1=0.415484 mm
L1=3.541880 mm
W2=0.224515 mm
L2=3.634570 mm
W3=0.101513 mm
L3=3.735550 mm
WL=0.058710 mm
LL=3.798950 mm

ADS -Microstrip TRLs(MSTEP) Layout

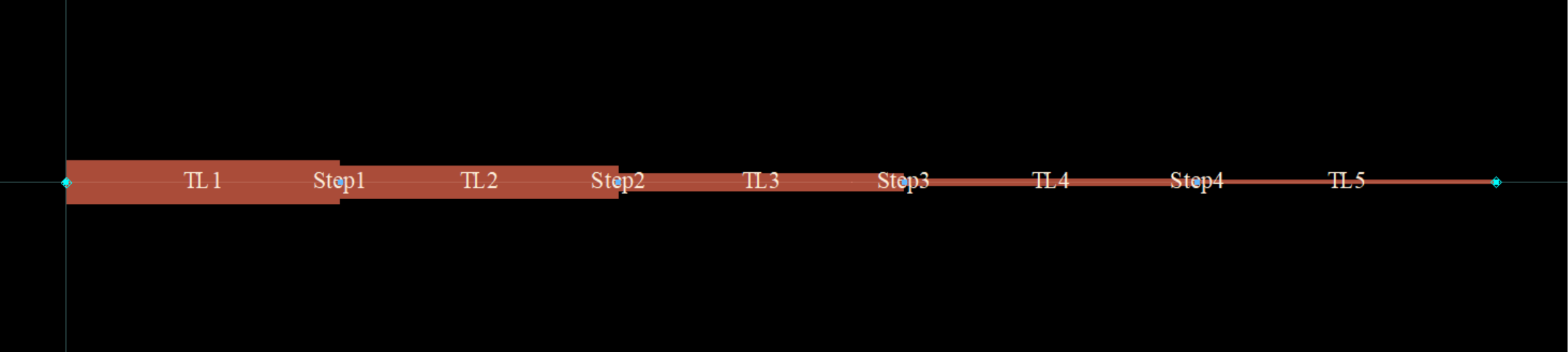

ADS -Microstrip TRLs(MSTEP)

S-Parameters vs. Frequency

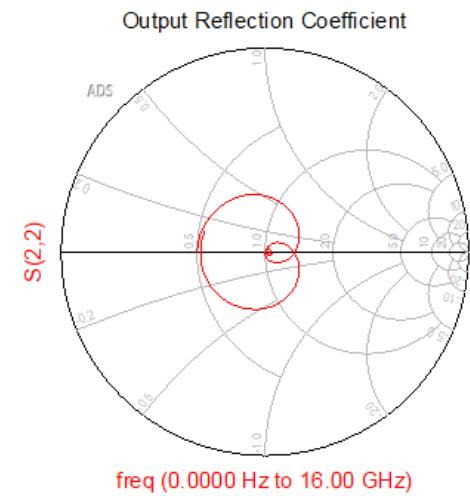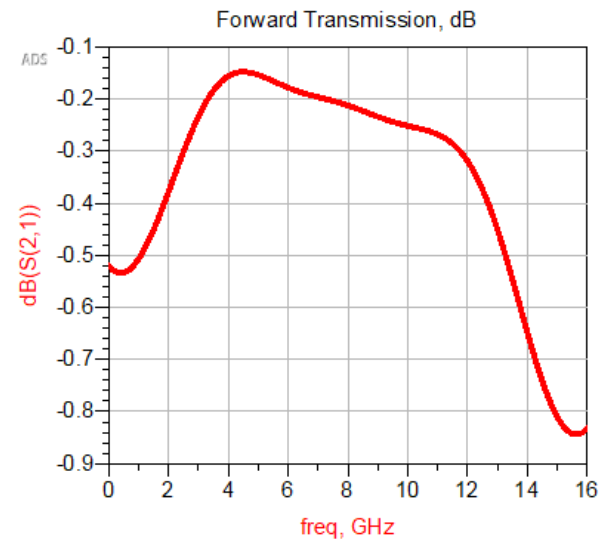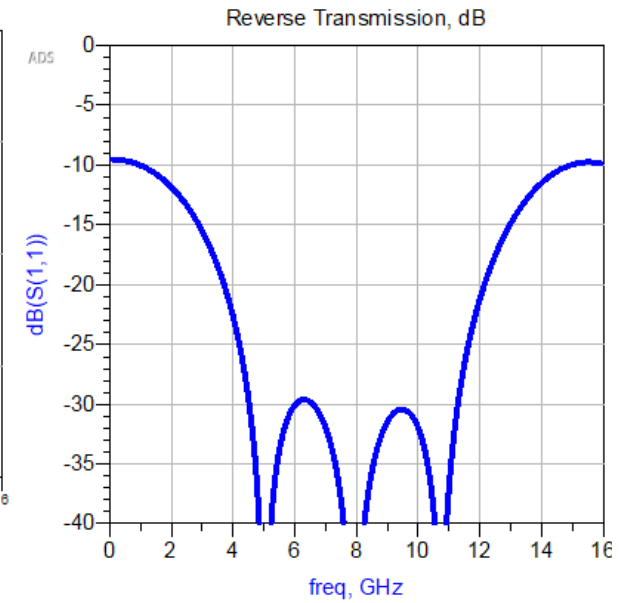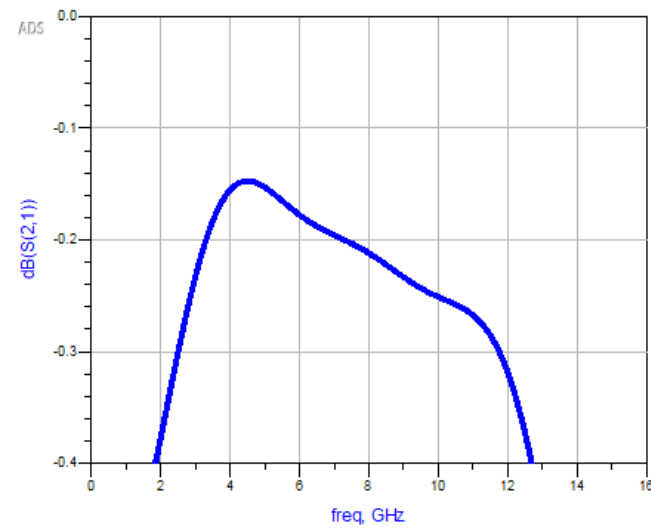

BUTTERWORTH

	Values	dB
S_{11}	-0.0000+j0.0006	-66.7879
S_{21}	0.0150-j0.9999	0.0000
S_{12}	0.0150-j0.9999	0.0000
S_{22}	0.0000-j0.0006	-66.7879

CHEBYSHEV

	Values	dB
S_{11}	0.0000+j0.0000	-166.9889
S_{21}	0.9999+j0.0242	0.0000
S_{12}	0.9999+j0.0242	0.0000
S_{22}	0.0000+j0.0000	-166.9889


ADS Microstrip

	Values	dB
S_{11}	0.0016-j0.0022	-50.5842
S_{21}	-0.0255-j0.9753	-0.2109
S_{12}	-0.0255-j0.9753	-0.2109
S_{22}	0.0032-j0.0008	-47.0322


ADS Microstrip Stepped

	Values	dB
S_{11}	0.0016-j0.0028	-48.4752
S_{21}	-0.0394-j0.9750	-0.2119
S_{12}	-0.0394-j0.9750	-0.2119
S_{22}	0.0035-j0.0003	-48.0703

On the same graph, plot $|S_{11}|$ (in dB) for the Butterworth simulated using MATLAB and the Chebyshev simulated using MATLAB. Employ a domain of 0 to 16 GHz and a range of -40 to 0 dB.

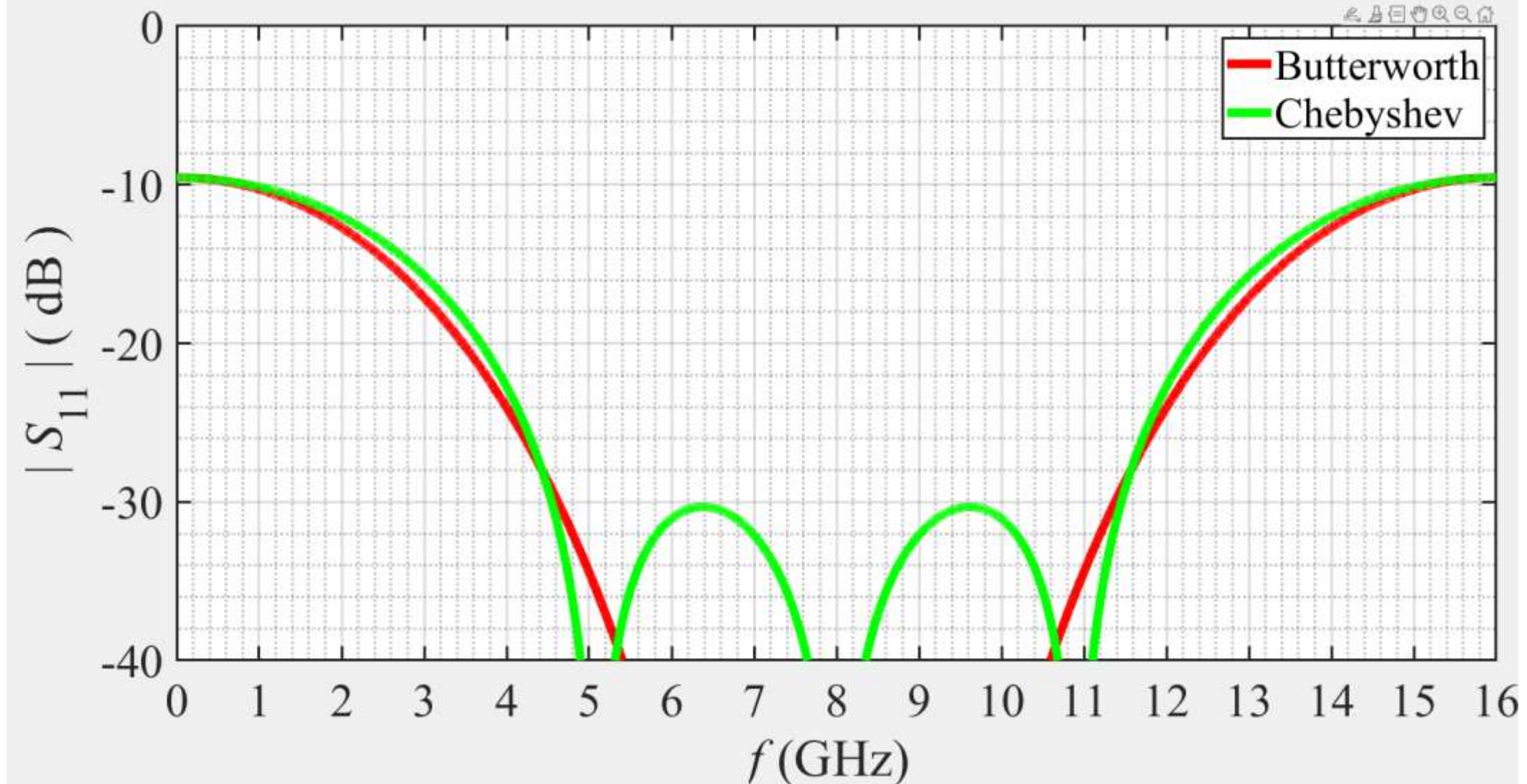


On the same graph, plot $|S_{21}|$ (in dB) for the Butterworth simulated using MATABL and the Chebyshev simulated using MATABL. Employ a domain of 0 to 16 GHz and a range of -0.25 to 0 dB.

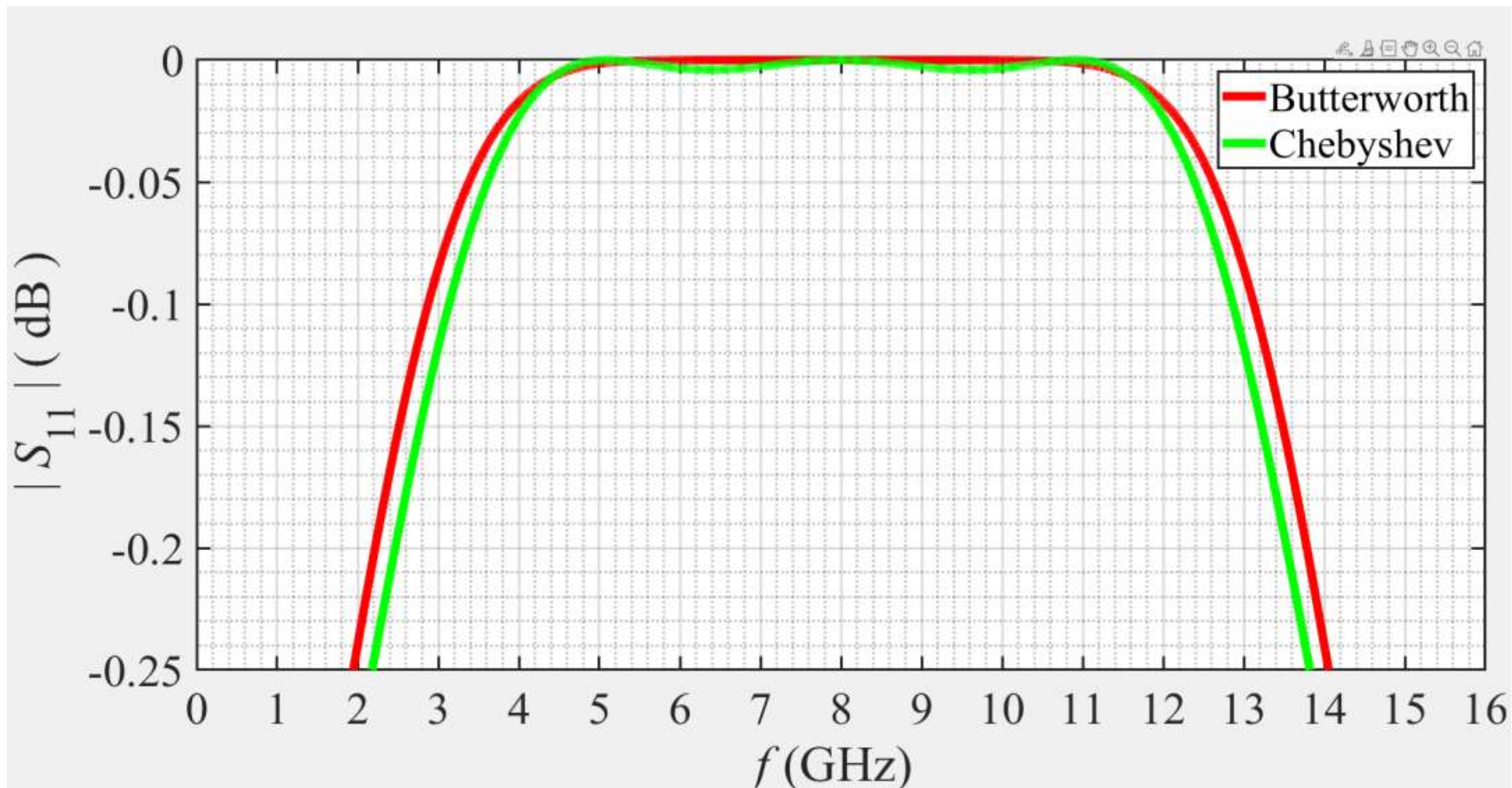

On the same graph, plot $|S_{11}|$ (in dB) for the Chebyshev simulated using MATLAB, ADS (Microstrip TRLs), and ADS (Microstrip TRLs with SD). Employ a range of -40 to 0 dB.

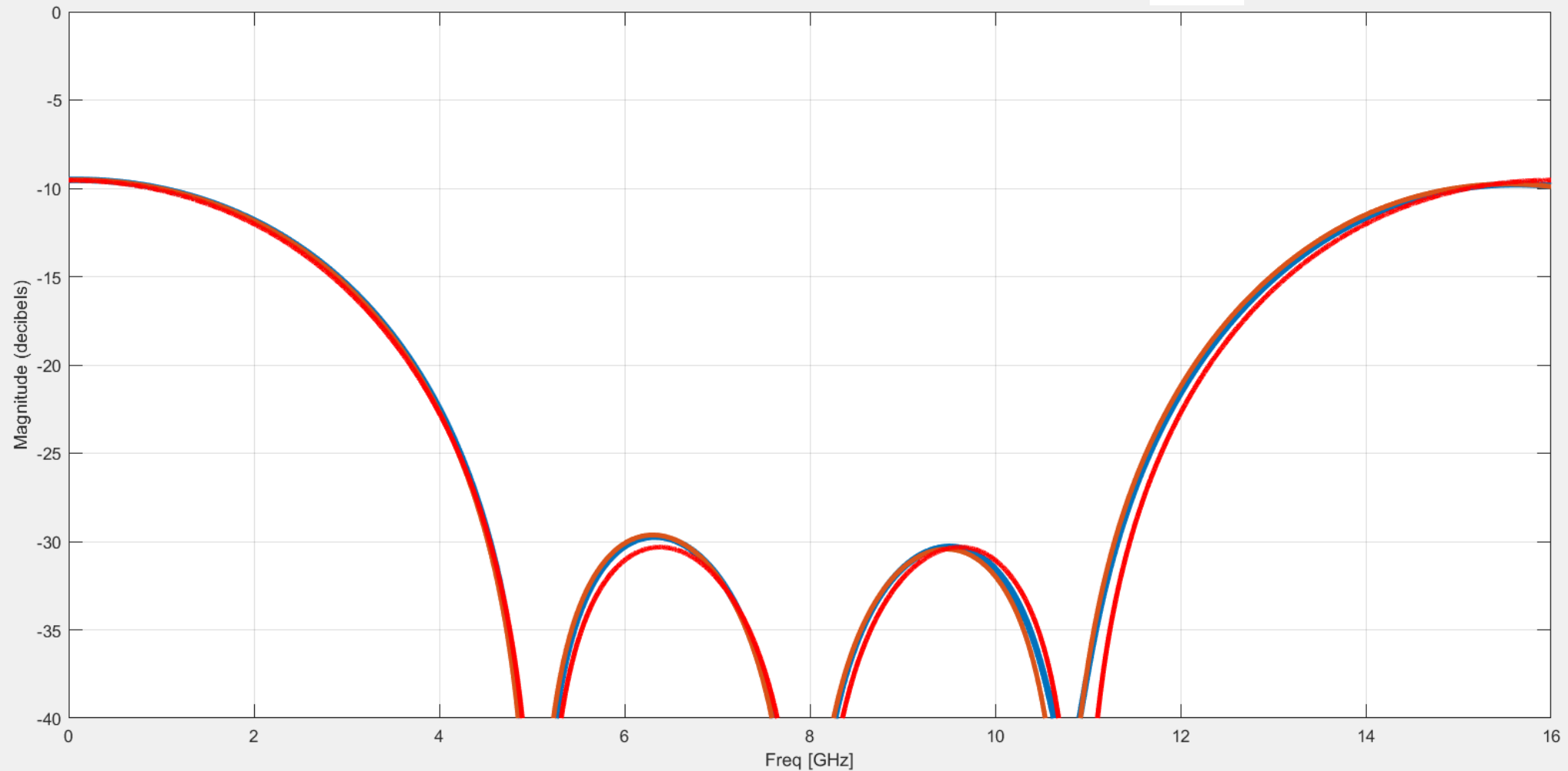— **MATLAB**
— **S_{11} Microstrip**
— **S_{11} Microstrip Stepped(MSTEP)**




On the same graph, plot $|S_{21}|$ (in dB) for the Chebyshev simulated using MATLAB, ADS (Microstrip TRLs), and ADS (Microstrip TRLs with SD). Employ a domain of 0 to 16 GHz and a range of -0.45 to 0 dB.

MATLAB

S_{21} Microstrip

S_{21} Microstrip Stepped(MSTEP)

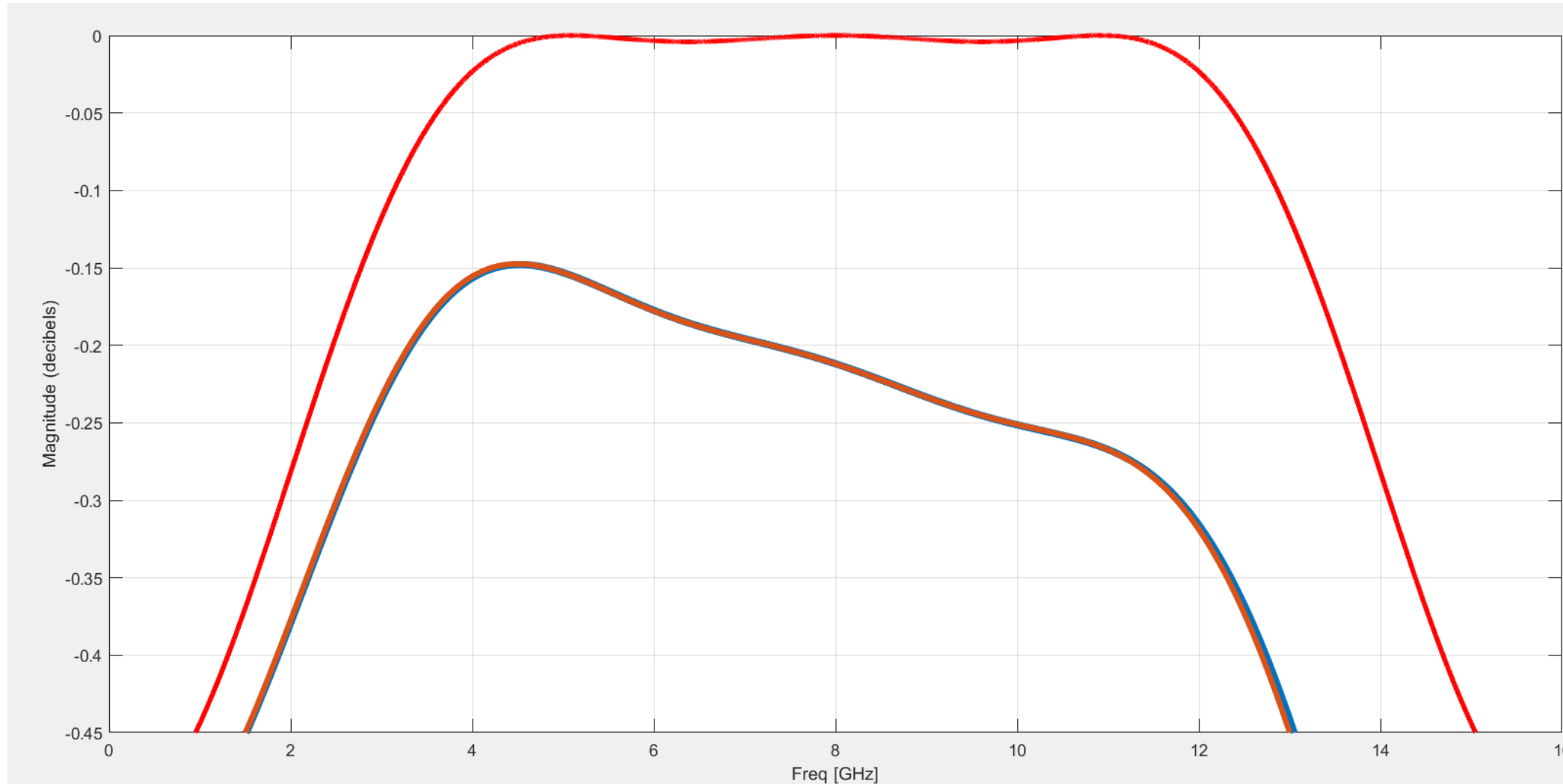

The End